

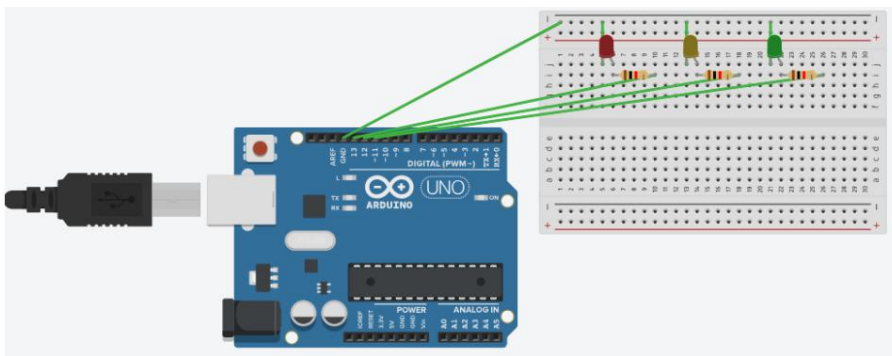


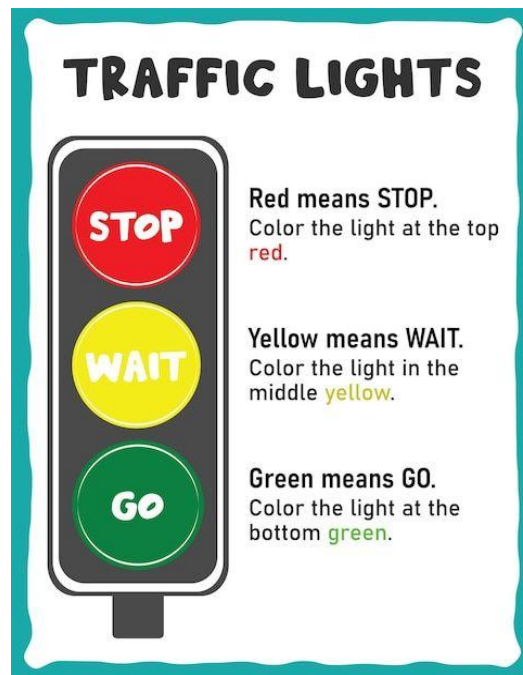

Name	Quantity	Component
1	1	Breadboard Small
D1	1	Red LED
D2	1	Yellow LED
D3	1	Green LED
R1 R2 R3	3	1 k Ω Resistor
U1	1	Arduino Uno R3

Schematic Diagram

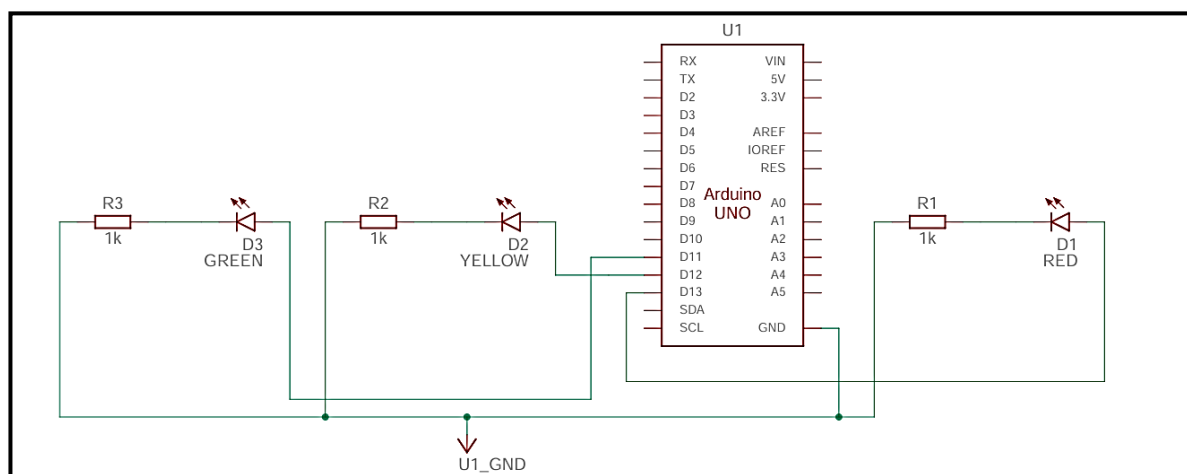

C++ code

```
void setup()
{
  pinMode(13, OUTPUT);
  pinMode(12, OUTPUT);
  pinMode(11, OUTPUT);
}
```

```
void loop()
{
  digitalWrite(13, HIGH);
  digitalWrite(12, LOW);
  digitalWrite(11, LOW);
  delay(1000);
  digitalWrite(13, LOW);
  digitalWrite(12, HIGH);
  digitalWrite(11, LOW);
  delay(1000);

  digitalWrite(13, LOW);
  digitalWrite(12, LOW);
  digitalWrite(11, HIGH);
  delay(1000);
}
```